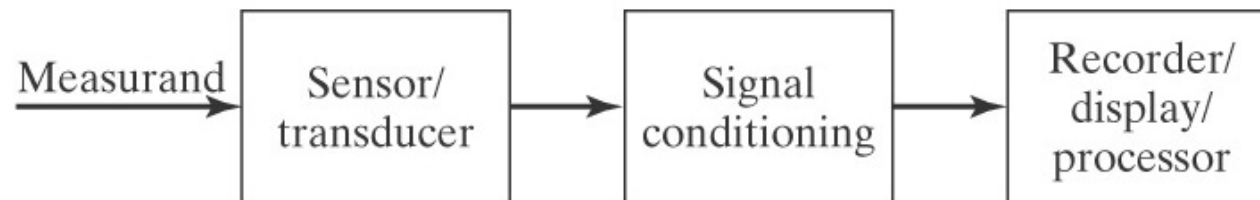

Signal Conditioning

Common Signal Conditioning Functions

- ❑ Amplification
- ❑ Attenuation
- ❑ Filtering
- ❑ Conversion (among voltage, current, and/or resistance)
- ❑ Differentiation
- ❑ Integration
- ❑ Linearization
- ❑ Frequency Analysis



Gain


- Gain is an expression of voltage amplification:

$$G = \frac{V_o}{V_i}$$


- Gain is often expressed in decibels:

$$G_{dB} = 20 \log_{10} \frac{V_o}{V_i}$$

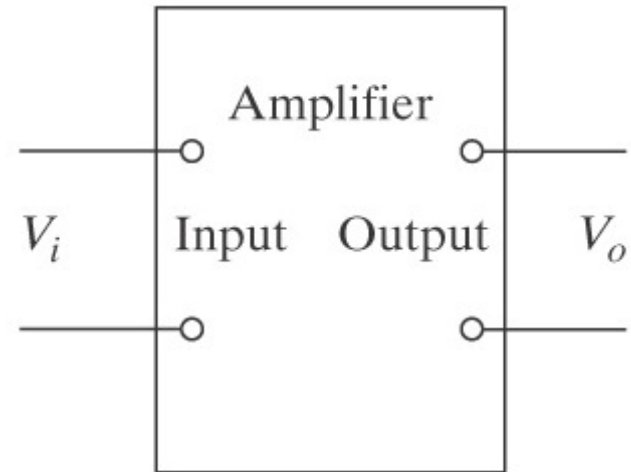- For example, $G = 1000$
corresponds to $G_{dB} = \underline{\hspace{1cm}} ?$



Bandwidth

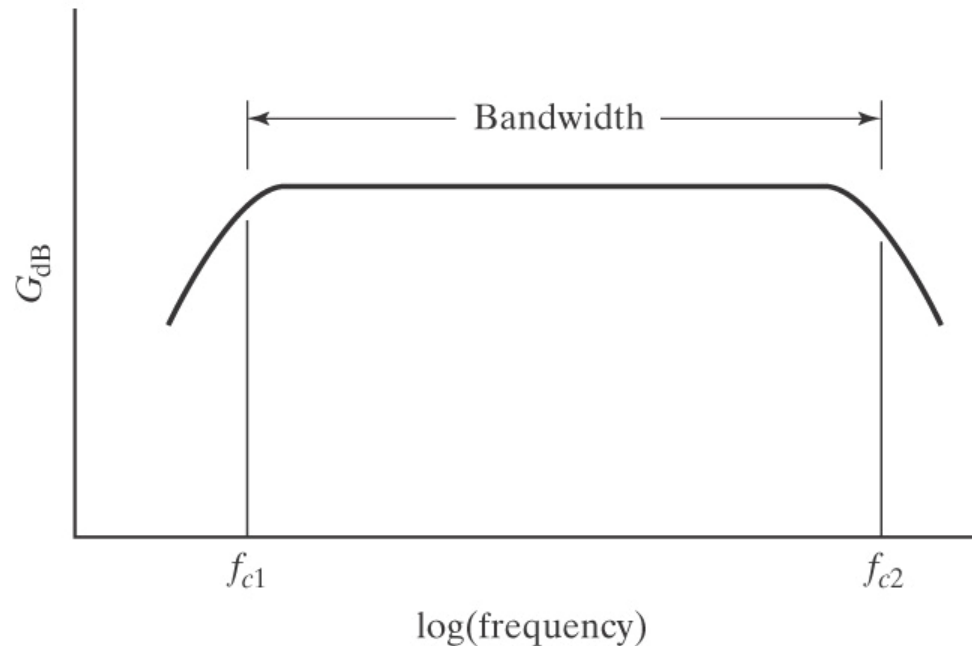

- ❑ Amplifiers do not provide constant gain throughout all operating frequencies.
- ❑ The **bandwidth** is frequency range in which gain is relatively constant.
- ❑ Beyond cut-off frequencies, amplified signals are likely to suffer from distortion.


Common-Mode Rejection

- ❑ Ideally, amplifiers should not produce any output if identical “common-mode” voltages are applied to both input terminals, and instead should amplify only inputs that are distinctly different (“differential-mode”).
- ❑ However, real amplifiers exhibit non-zero output even for common-mode voltages.
- ❑ A high-quality amplifier should have a large common-mode rejection ratio:

$$\text{CMRR} = 20\log_{10} \frac{G_{diff}}{G_{cm}}$$

- ❑ Commercial amplifiers can readily have $\text{CMRR} > 100$ dB, so $G_{diff}/G_{cm} = \underline{\hspace{2cm}}$?

Loading Problems

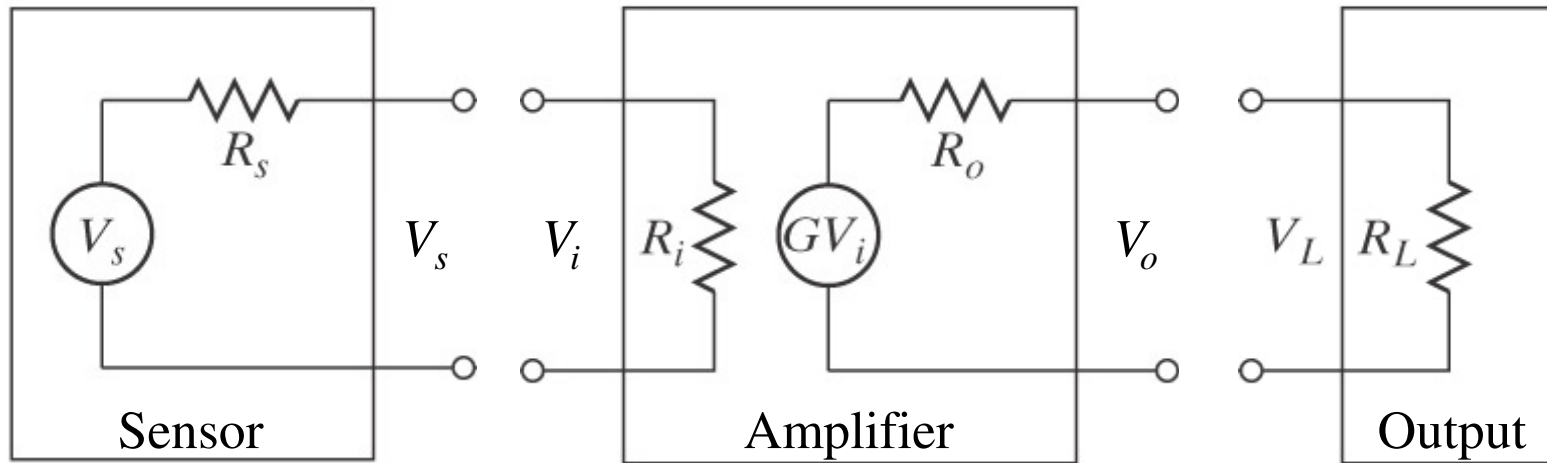


- ❑ Connecting an amplifier to a sensor can change what would otherwise have been the original signal V_s , because a new circuit loop is made. Likewise a problem at the output. Circuit analysis shows:


$$V_i = \frac{R_i}{R_s + R_i} V_s$$

$$V_L = \frac{R_L}{R_o + R_L} GV_i$$

Examples of Operational Amplifiers

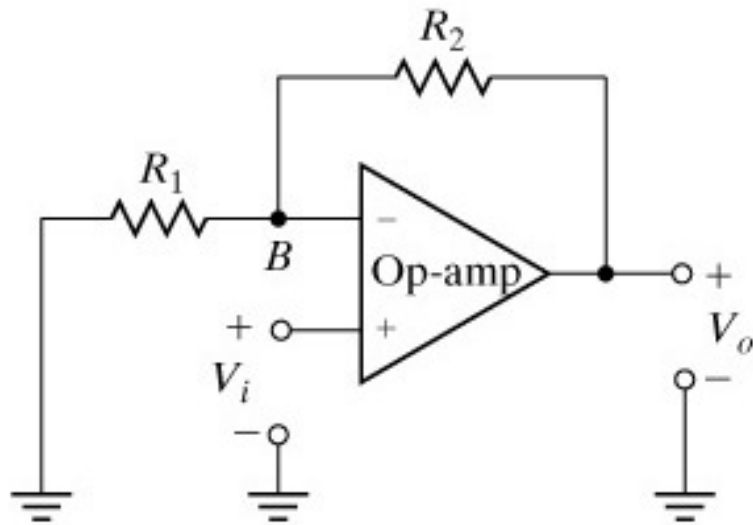

$$G = 1 + \frac{R_2}{R_1}$$

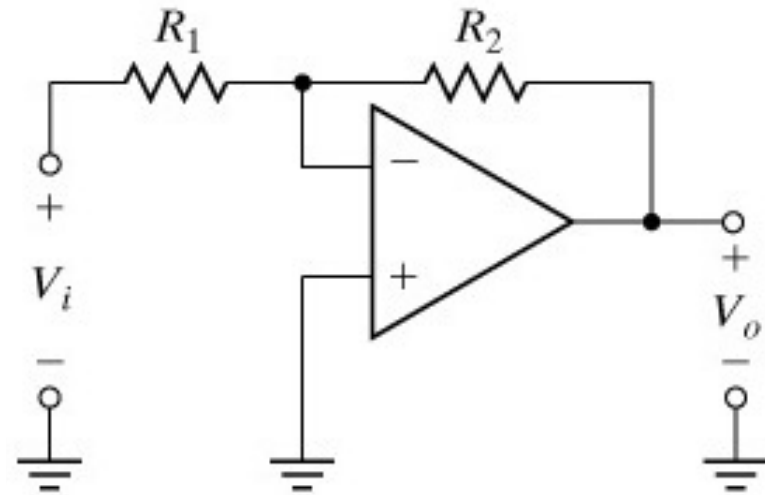

$$G = -\frac{R_2}{R_1}$$


- ❑ Commercial op-amps readily can have gain $> 10^5$, CMRR near 100 dB, input impedance $> 10^5 \Omega$, and output impedance $< 100 \Omega$. Why are these good?

Signal Attenuation

- ❑ The most straightforward way to attenuate (reduce) a voltage that is higher than desirable for measurement electronics is to use a voltage divider:

$$V_o = \frac{R_2}{R_1 + R_2} V_i$$

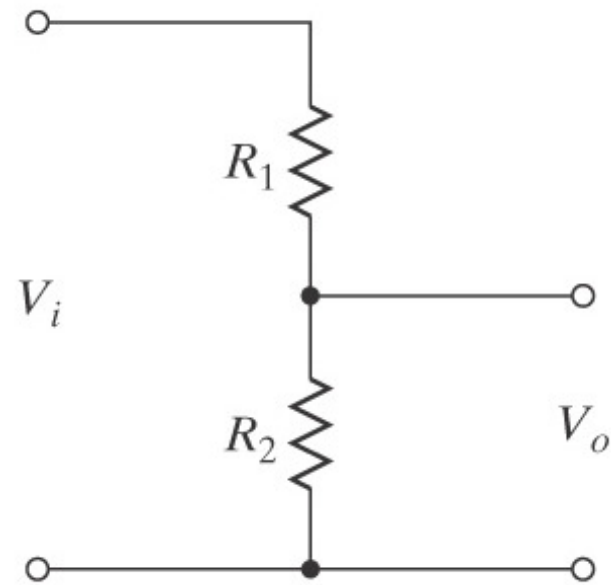- ❑ A drawback is that the resistors of the voltage divider cause loading effects.



Signal Filtering

- ❑ Filtering is often needed to remove selected ranges of frequencies in time-varying voltage signals.
- ❑ The most intuitive and common scenario that demands filtering is the rejection of high-frequency noise.
- ❑ A low-pass filter attenuates high frequencies, a high-pass filter attenuates low frequencies, and a band-pass filter attenuates both low and high frequencies.

