


Physics 51 Proficiency Test 3(sample) (Time: 10 minutes) **25 points**
By Todd Sauke

Name _____

Section # _____

What is the equivalent resistance between the points A and B in the circuit at right ?

_____ Ω

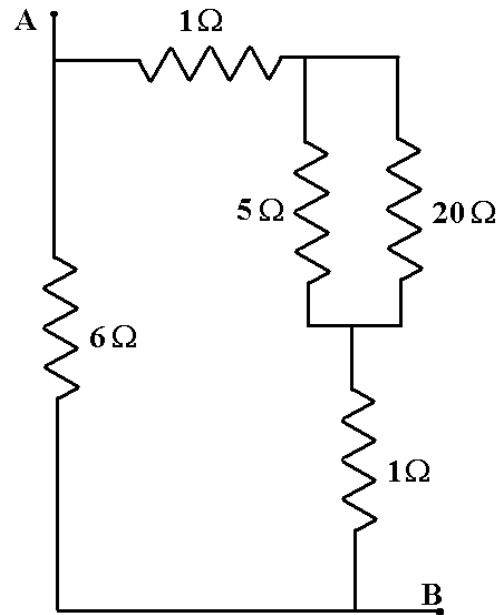

What is the equivalent capacitance between the points C and D in the circuit at right ?

_____ μF

